

## Sign Conventions and Laws

### Ohm's Law

$$V = +iR \quad (i \text{ enters } V+)$$

$$V = -iR \quad (i \text{ enters } V- // i \text{ leaves } V+)$$

### KVL

$$\sum V = 0V$$

(+) if  $i$  enters (+) terminal

(-) if  $i$  enters (-) terminal

### KCL

$$\sum i = 0A$$

$$i_{entering} = i_{leaving} \text{ at a node}$$

### Power

$$P = +iV \quad (i \text{ enters } +)$$

$$P = -iV \quad (i \text{ enters } -)$$

(+) Power = Power Absorbed

(-) Power = Power Delivered

### Nodal Ohm's Law

$$i = \frac{V_A - V_B}{R} \quad V_A - V_B \text{ (Tail - Head)}$$

### Superposition

- Check for Linear
- Keep one source
- Solve for values
- Sum results

### Resistors in Series

- Current is the same across the resistors

#### Equivalent Resistance

$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

#### Voltage Divider

$$V_n = +V_s \frac{R_n}{R_{eq}} \quad (+ \text{ terminals face each other})$$

$$V_n = -V_s \frac{R_n}{R_{eq}} \quad (+ \text{ and } - \text{ terminals face each other})$$

### Resistors in Parallel

- Voltage is the same across all branches

#### Req

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$$

For two resistors:

$$R_{eq} = \frac{R_1(R_2)}{R_1 + R_2}$$

#### Current Divider

$$i_n = +i_s \frac{R_{eq}}{R_n} \quad (i \text{ is the same direction})$$

$$i_n = -i_s \frac{R_{eq}}{R_n} \quad (i \text{ is opposite direction})$$

With two resistors:

$$i_1 = i_s \frac{R_2}{R_1 + R_2}$$

### Thevenin/ Norton Equivalents

$$V_T = V_{OC}$$

$$R_T = R_{eq}$$

$$i_N = \frac{V_T}{R_T}$$

With a Dependent Source:

$V_T$  and  $i_N$  is the same

$$R_{eq} = \frac{V_T}{i_N}$$